

Lab 01: SPICE

Part (1)

(1)

```
Voltage Divider Netlist
* Any text after the asterisk '*' is ignored by SPICE
* Voltage Divider
V1 1 0 12
R1 1 2 1k
R2 2 0 2k
* Perform operating point analysis
*** add line here ***
.OP
*** add line here ***
.END
```

```
Voltage Divider Netlist

--- Operating Point ---


V(1):      12          voltage
V(2):      8           voltage
I(R2):      0.004      device_current
I(R1):      0.004      device_current
I(V1):     -0.004      device_current
```

(2)

```
Simple RC Circuit

* Circuit Description
|
* Parameters
*** add line here ***
.PARAM CPAR 500p
* Signal sources
*** complete this line *** (0V 1V 0 100n 100n 10u 20u)
Vtran 1 0 PULSE(0V 1V 0 100n 100n 10u 20u)
* Circuit elements
R1 1 2 1k
C1 2 0 {CPAR}

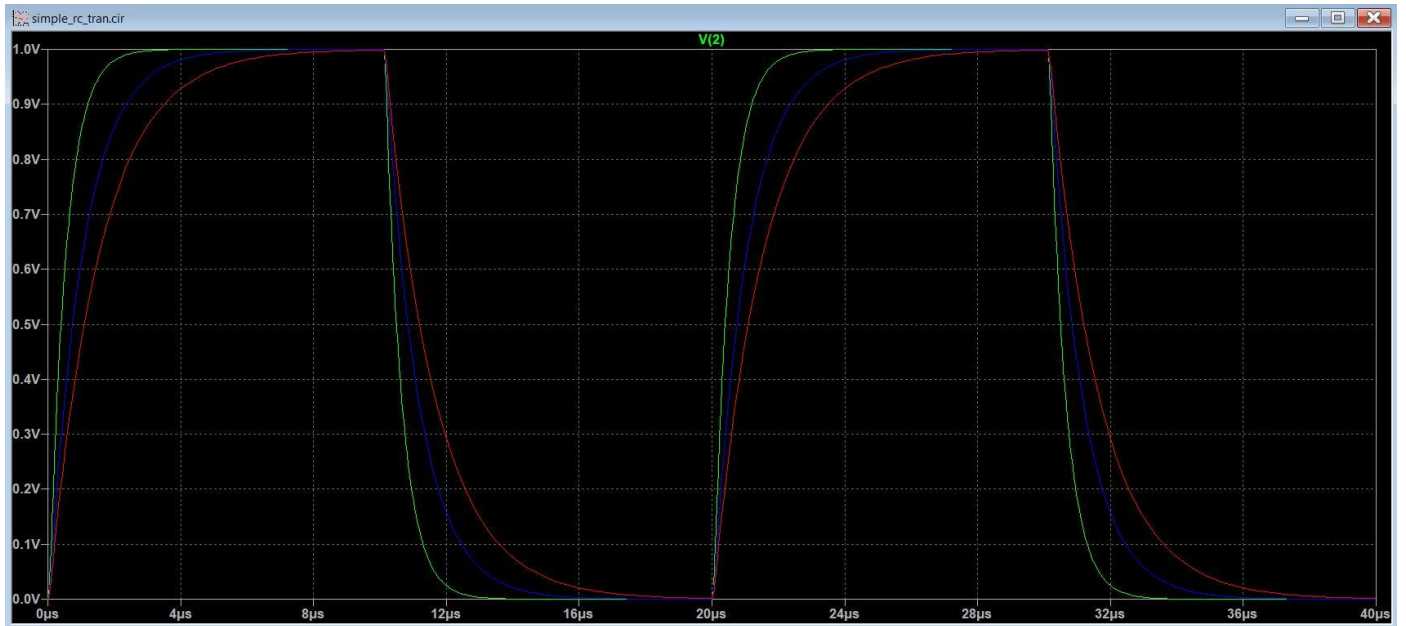* Initial conditions
* Analysis request
* Run transient for 40us with 100ns step
*** add line here ***
.TRAN 100ns 40us
* Use parametric sweep for CPAR: 500p:500p:1.5n
*** add line here ***
.STEP PARAM CPAR 500p 1.5n 500p
* Measure rise time from 10% to 90%
.MEAS TRAN TRISE
+ TRIG when v(2) = 0.1 CROSS = 1
*** add line here ***
+ TARG when v(2) = 0.9 CROSS = 1
*** add line here ***
.END
```



Circuit: Simple RC Circuit

```
.OP point found by inspection.
.step cpar=5e-010
.step cpar=1e-009
.step cpar=1.5e-009
```

Measurement: trise

step	trise	FROM	TO
1	1.09912e-006	1.03619e-007	1.20274e-006
2	2.19839e-006	1.56143e-007	2.35454e-006
3	3.29638e-006	2.08794e-007	3.50517e-006

(3)

Simple RC Circuit

* Circuit Description

* Parameters

*** add line here ***

.PARAM CPAR 500p

* Signal sources

*** add line here ***

Vac 1 0 AC 1V

* Circuit elements

R1 1 2 1k

C1 2 0 {CPAR}

* Analysis request

* Run ac sweep from 1Hz to 100MEG with 10 pts per decade

*** add line here ***

.AC DEC 10 1Hz 100MEG

* Use parametric sweep for CPAR: 500p:500p:1.5n

*** add line here ***

.STEP PARAM CPAR 500p 1.5n 500p

* Output request

.PRINT AC V(1) V(2)

.PLOT AC V(1) V(2)

* Measure the peak

.MEAS AC PEAK max mag(V(2))

* Measure bandwidth using PEAK/sqrt(2)


.MEAS AC BW

*** add line here ***

+ WHEN mag(V(2)) = PEAK/sqrt(2)

*** add line here ***

.END

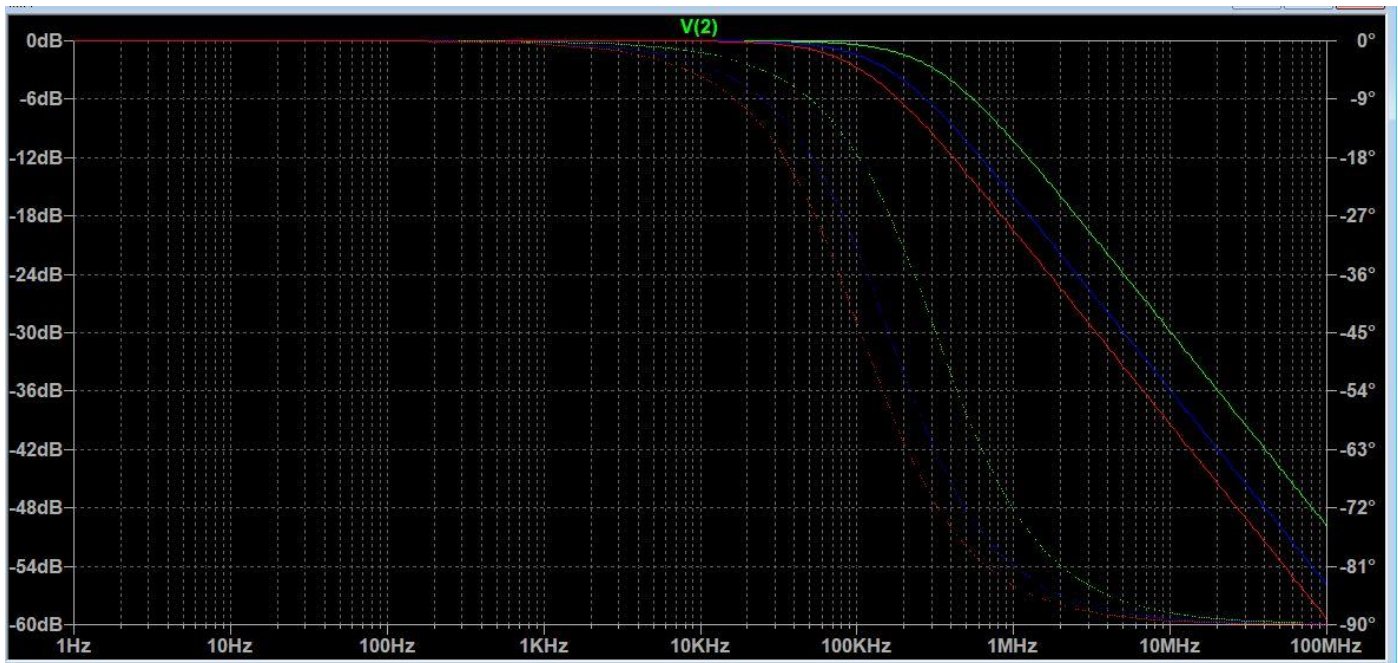

Circuit: Simple RC Circuit

```
.step cpar=5e-010
.step cpar=1e-009
.step cpar=1.5e-009
```

Measurement: peak

step	MAX(mag(v(2)))	FROM	TO
1	(-4.28644e-011dB, 0°)	1	1e+008
2	(-1.71454e-010dB, 0°)	1	1e+008
3	(-3.8577e-010dB, 0°)	1	1e+008

Measurement: bw

step	mag(v(2))=peak/sqrt(2)
1	318461
2	159204
3	106411

Part (2)

(1)

* Non-ideal Op-amp (small signal) Subcircuit

*

* Subcircuit Description

*

.SUBCKT small_signal_OPAMP IN+ IN- OUT

* connections: | | |

* +ve input | |

* -ve input |

* output

Ginput 0 4 IN+ IN- 10

Iopen1 IN+ 0 0A ; redundant connection made at +ve input terminal

Iopen2 IN- 0 0A ; redundant connection made at -ve input terminal

R1 4 0 1k

C1 4 0 159.155n

Eoutput OUT 0 4 0 1

.ENDS small_signal_OPAMP

.END

Circuit parameters calculations:

$$A_o \omega_B = \omega_t \rightarrow (10^4) f_B = 10 \text{ MHz} \rightarrow f_B = 1 \text{ kHz}$$

$$A_o = G_m R_1 = 10^4 \rightarrow (1)$$

$$\omega_B = 2\pi f_B = 1/R_1 C_1 \rightarrow 2\pi(1 \text{ kHz}) = 1/R_1 C_1 \rightarrow (2)$$

Let $R_1 = 1 \text{ K}\Omega$, then solve (1) & (2) together:

$C_1 = 159.155 \text{ nF}$, $G_m = 10$

(2)

```
Non-inverting Amplifier
*
* Subcircuit Description
*
.INC small_signal_OPAMP.cir
*
* Circuit Description
*
* Signal source
Vin 3 0 DC 1
*
* Circuit elements
R1 0 2 1k
Rf 2 1 9k
XOPAMP1 3 2 1 small_signal_OPAMP
*
* Analysis Request
*
.TF V(1) Vin
.END
```

Non-inverting Amplifier		
--- Transfer Function ---		
Transfer_function:	9.99001	transfer
vin#Input_impedance:	1e+020	impedance
output_impedance_at_V(1):	0	impedance


An ideal op-amp has:

- an infinite input impedance (shown in the output 1e+020 referring to a very high input impedance)
- Output impedance equals zero (as shown in the output)

The gain of the non-inverting amplifier is $A_v = 1 + R_f/R_1 = 1 + 9/1 = 10$ for ideal op-amp.

For non-ideal op-amp, $A_v = (1 + R_f/R_1)(1 - (1 + R_f/R_1)/A_0) = 9.99$ (as shown in the output).

(3)

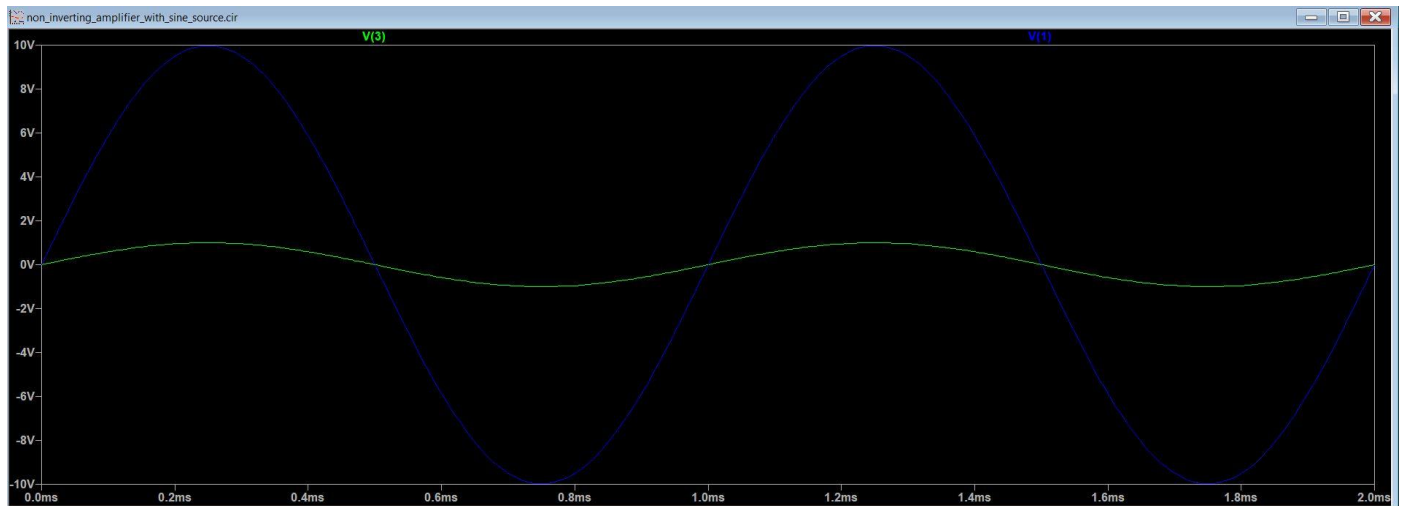

(V_{sig} in green and V_{out} in blue)


```

Non-inverting Amplifier
*
* Subcircuit Description
*
.INC small_signal_OPAMP.cir

*|
* Circuit Description
*
* Parameters
.PARAM PERIOD = 1m

* Signal source
Vin 3 0 SIN(0 1 1k 0 0)

* Circuit elements
R1 0 2 1k
Rf 2 1 9k
XOPAMP1 3 2 1 small_signal_OPAMP

*
* Analysis Request
*
.TRAN {PERIOD/50} {2*PERIOD}

* Output request
.PRINT TRAN V(1) V(2) V(3)
.PLOT TRAN V(1) V(2) V(3)

* Measure the peak
.MEAS TRAN Vout_PEAK max ABS(V(1))
.MEAS TRAN Vsig_PEAK_+node max ABS(V(3))
.MEAS TRAN Vsig_PEAK_-node max ABS(V(2))

.END
vout_peak: MAX(abs(v(1)))=9.98038 FROM 0 TO 0.002
vsig_peak_+node: MAX(abs(v(3)))=0.999081 FROM 0 TO 0.002

```


(4)

Voltage gain = $9.98038/0.999081 = 9.98956$

Hand analysis	TF analysis	TRAN analysis
9.99	9.99001	9.98956

The TF is almost the same as the hand analysis. In contrast, the TRAN analysis is lower because it uses a frequency 1kHz, and the gain decreases with frequency.

(5)

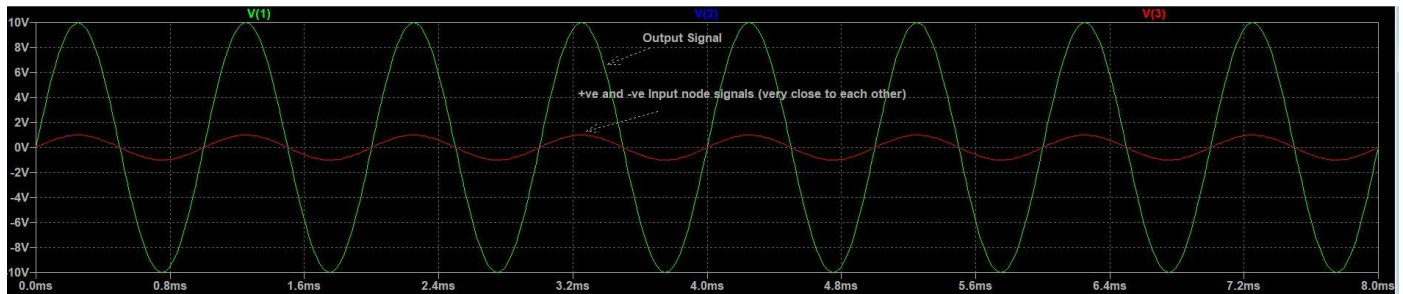


```

differential_input_peak: MAX(abs(v(3)-v(2)))=0.00143945 FROM 0 TO 0.002


```

differential input waveform

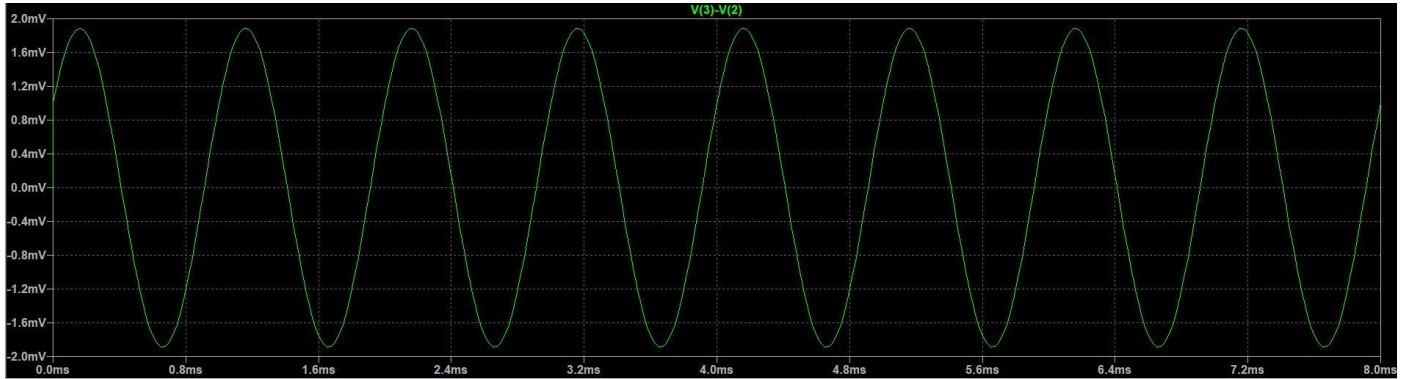

The amplitude of the differential input is $0.999081 - 0.998038 = 1\text{mV}$ because $V_{in} = (V_{out})/(A_o/\sqrt{2}) = 10/(10^4/\sqrt{2}) = 1.414\text{mV}$

(6)

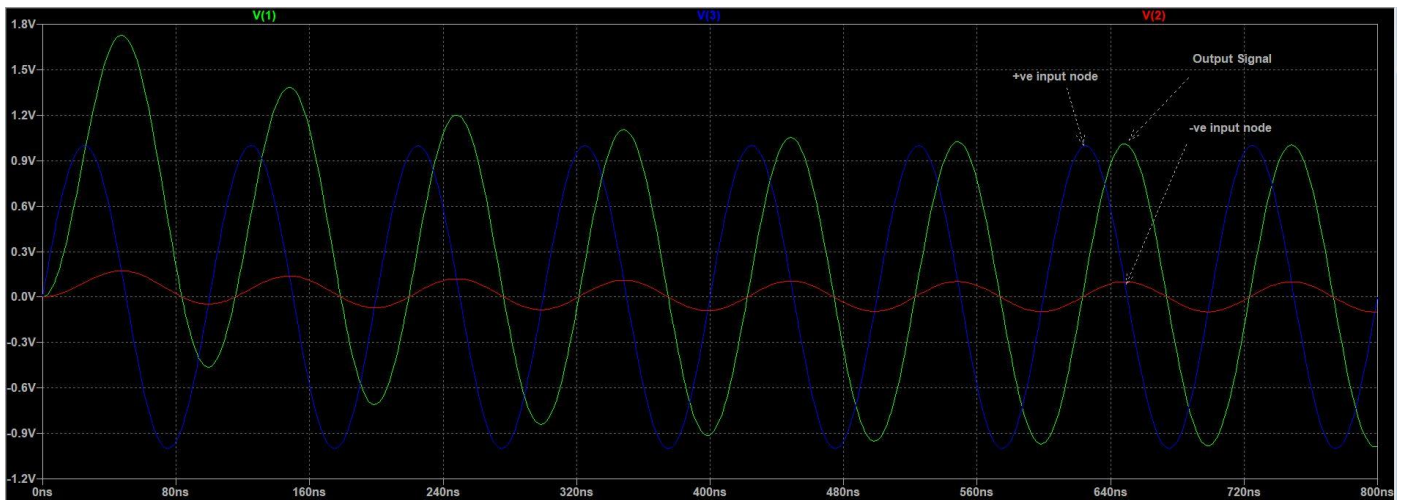

```
Non-inverting Amplifier
*
* Subcircuit Description
*
.INC small_signal_OPAMP.cir

*
* Circuit Description
*
* Parameters
*.PARAM PERIOD = 1m
.PARAM PERIOD = 100n ; For input frequency equal to the UGF

* Signal source
*Vin 3 0 SIN(0 1 1k 0 0)
Vin 3 0 SIN(0 1 10MEG 0 0) ; Input frequency equal to the UGF
* Circuit elements
R1 0 2 1k
Rf 2 1 9k
XOPAMP1 3 2 1 small_signal_OPAMP

*
* Analysis Request
*
.TRAN {PERIOD/50} {8*PERIOD}

* Output request
.PRINT TRAN V(1) V(2) V(3)
.PLOT TRAN V(1) V(2) V(3)

* Measure the peak
.MEAS TRAN Vout_PEAK max ABS(V(1))
.MEAS TRAN Vsig_PEAK_+node max ABS(V(3))
.MEAS TRAN Vsig_PEAK_-node max ABS(V(2))
.MEAS TRAN Differential_input_PEAK max ABS(V(3)-V(2))
.END
```

```
SPICE Error Log: D:\Summer2022\AMS Course\ams_labs_pdf\lab1\non_inverting_amplifier_with_sine_s
Circuit: Non-inverting Amplifier

.OP point found by inspection.

vout_peak: MAX(abs(v(1)))=1.72696 FROM 0 TO 8e-007
vsig_peak_+node: MAX(abs(v(3)))=0.999884 FROM 0 TO 8e-007
vsig_peak_-node: MAX(abs(v(2)))=0.172696 FROM 0 TO 8e-007
differential_input_peak: MAX(abs(v(3)-v(2)))=1.05709 FROM 0 TO 8e-007

Date: Fri Aug 05 23:33:24 2022
Total elapsed time: 0.275 seconds.

tnom = 27
temp = 27
method = modified trap
totiter = 2082
traniter = 2082
tranpoints = 1042
accept = 1042
rejected = 0
matrix size = 6
fillins = 1
solver = Normal
Matrix Compiler1: 182 bytes object code size 0.2/0.2/[0.1]
Matrix Compiler2: off [0.1]/0.4/0.2
```

Differential input waveform:



The amplitude of the **differential** input signal is 1V because at UGF the gain is 1, so because $V_{in} = V_{out}/A_o = 1/1 = 1V$

Note that the reported peak value of the output signal is incorrect due to the dc shift that fades with time.

(7)



```

Non-inverting Amplifier
*
* Subcircuit Description
*
.INC small_signal_OPAMP.cir

*
* Circuit Description
*
* Parameters
.PARAM RF_PAR 9k

* Signal source
Vac 3 0 AC 1V

* Circuit elements
R1 0 2 1k
RF 2 1 {RF_PAR}
XOPAMP1 3 2 1 small_signal_OPAMP

* Analysis Request
*
.AC DEC 10 1Hz 100MEG
.STEP PARAM RF_PAR LIST 9k 4k

* Output request
.PRINT TRAN V(1) V(2) V(3)
.PLOT TRAN V(1) V(2) V(3)

* Measure the peak
.MEAS AC DC_GAIN max mag(V(1))
.MEAS AC CUTOFF_FREQ WHEN mag(V(1)) = DC_GAIN/sqrt(2)
.MEAS AC UGF WHEN mag(V(1)) = 1

.END

```

```

.step rf_par=4000
.step rf_par=9000

```

Measurement: dc_gain

step	MAX(mag(v(1)))	FROM	TO
1	(13.9751dB, 0°)	1	1e+008
2	(19.9913dB, 0°)	1	1e+008

Measurement: cutoff_freq

step	mag(v(1))=dc_gain/sqrt(2)
1	2.00142e+006
2	1.00107e+006

Measurement: ugf

step	mag(v(1))=1
1	9.83357e+006
2	9.95973e+006

(8)

If you increase the input amplitude in AC analysis and transient analysis, do you expect to see clipping in the output? Why?

No, because our model doesn't include this large-signal non-ideality.

(9)

For $R_f = 9k$

	DC gain	Cutoff frequency	UGF
Hand analysis	10 (assuming ideal op-amp) 9.99 (taking the gain error into account)	UGF/DC_Gain = 1MHz	= Closed-loop UGF = open-loop UGF = 10MHz

AC analysis	19.9913dB =9.989989	1MHz	9.95973MHz
-------------	------------------------	------	------------

For $R_f = 4k$

	DC gain	Cutoff frequency	UGF
Hand analysis	5(assuming ideal op-amp)	UGF/DC_Gain = 2MHz	= Closed-loop UGF = open-loop UGF = 10MHz
AC analysis	13.9751dB = 4.9975	2MHz	9.83357MHz

Comment: the closed-loop amplifier decrease the dc gain and increases the cutoff frequency such that the gain-bandwidth product is the same, so by changing the feedback resistance, the DC gain and cutoff frequency change while UGF is the same.

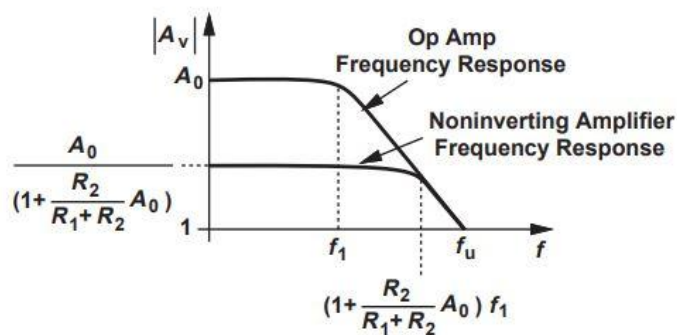


Figure 8.37 Frequency response of open-loop op amp and closed-loop circuit.