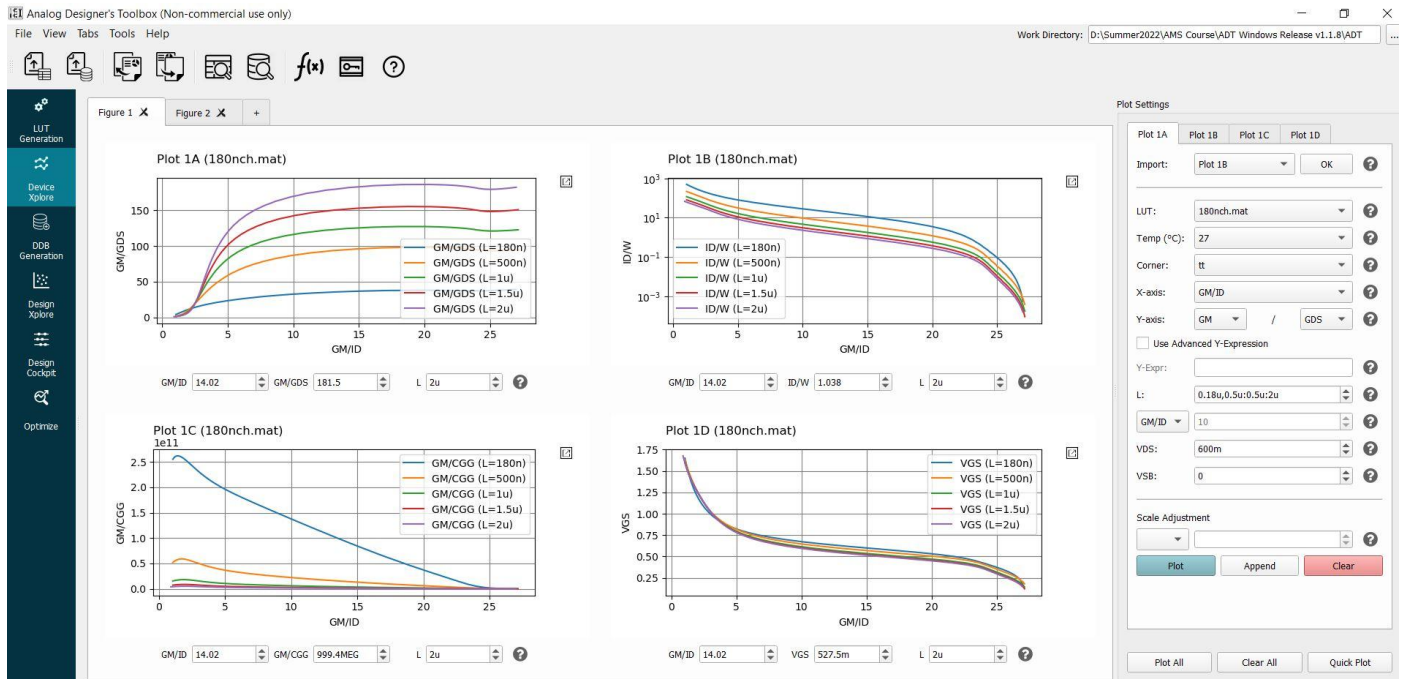



# Lab 04: Analog Design Automation

## Part 1: (index 1)


For nmos,



For pmos,

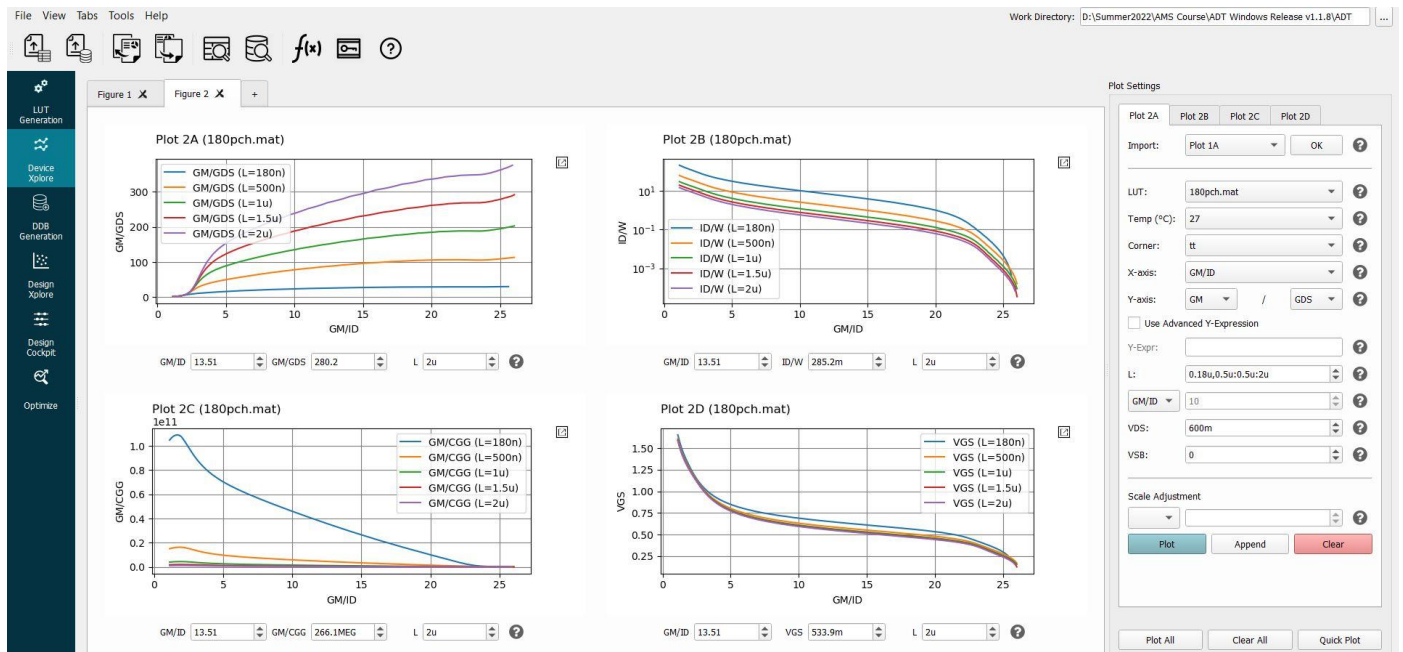

(index 2)

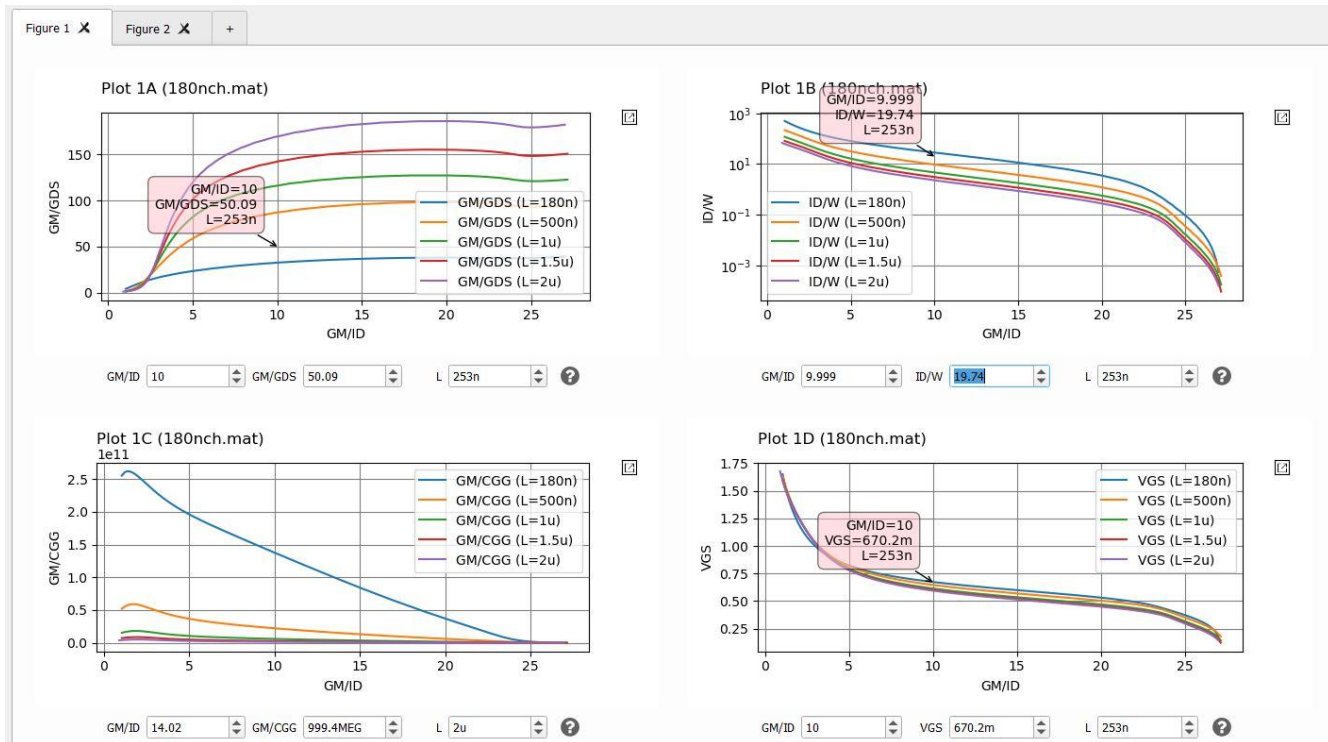

$L = 253 \text{ nm}$

$V_{GS} = 670.2 \text{ mV}$

$I_{D/W} = 19.74 \text{ A/m}$

$I_D = 19.74 * (5u) = 98.7 \text{ uA}$

**(index 3)**




Command Window

```
VGS = 0.67
ID = 9.52e-05
fx >>
```

	ADT	Matlab
$V_{GS}$	670.2 mV	670 mV
$I_D$	98.7 uA	95.2 uA

**(index 4)**



For the input pair (nmos),

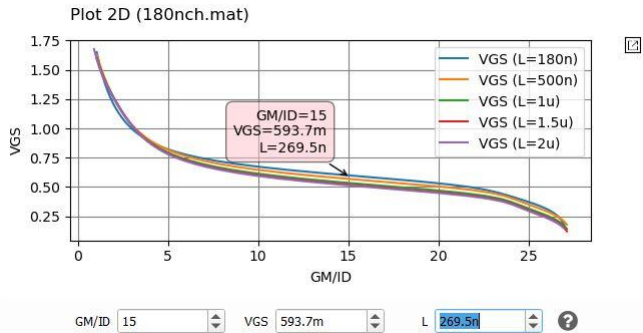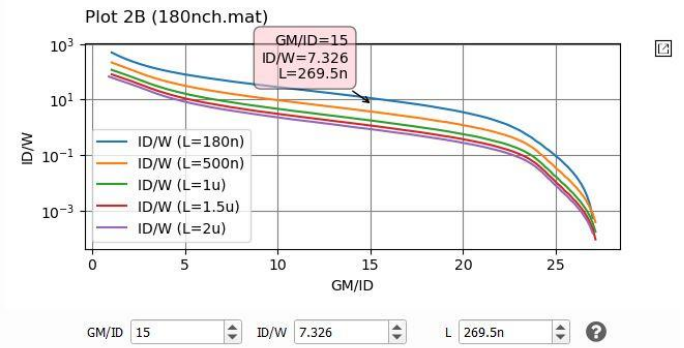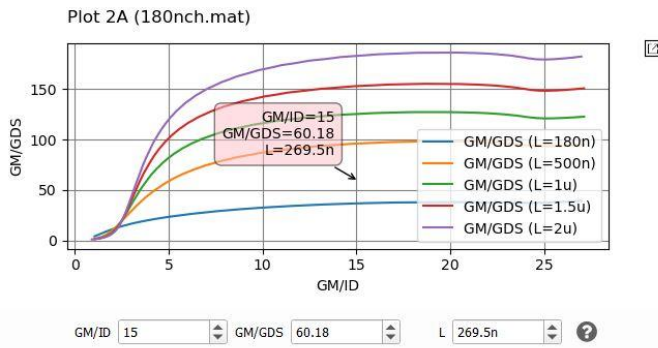

$gm_{1,2} = 314.16 \mu S$ ,  $ro_{1,2} = 191.439 \text{ k}\Omega$ ,  $(gm_{1,2})(ro_{1,2}) = 60.14244$

**$L_{1,2} = 269.5 \text{ nm}$ ,  $W_{1,2} = 2.859 \mu m$**



For the current mirror load (pmos),

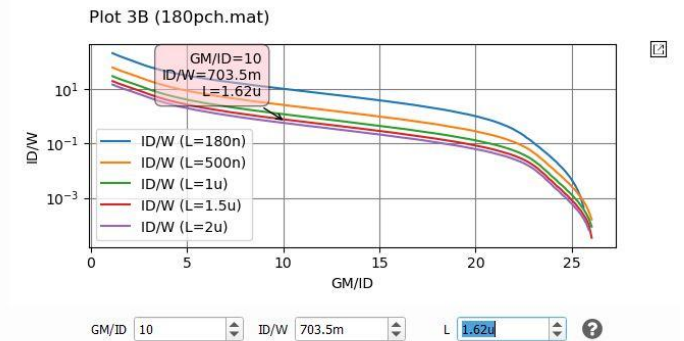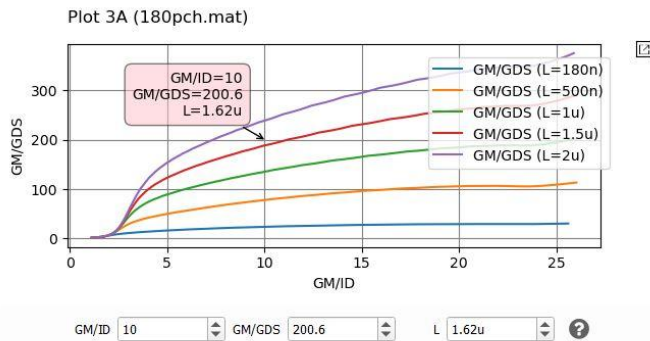

$gm_{3,4} = 209.44 \mu S$ ,  $ro_{3,4} = 5 \times (191.439) \text{ k}\Omega$ ,  $(gm_{3,4})(ro_{3,4}) = 200.475$

**$L_{3,4} = 1.62 \mu m$ ,  $W_{3,4} = 29.77 \mu m$**

For the tail current source (nmos),

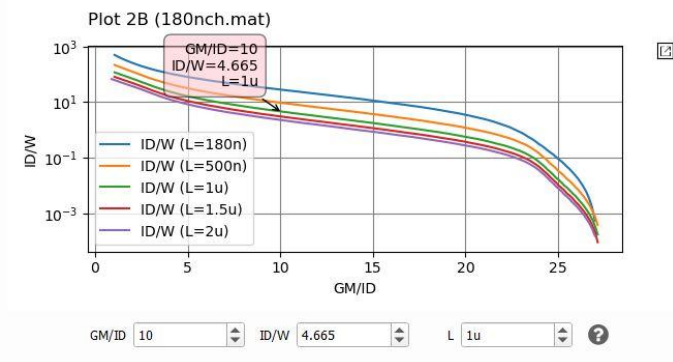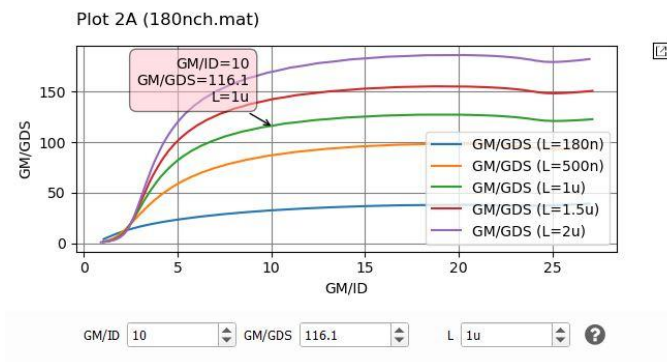

$L_5 = 1 \text{ } \mu\text{m}$ ,  $ID/W = 4.665$ ,  $W_5 = 8.979 \text{ } \mu\text{m}$

**gm/ID = 15 for the input pair and gm/ID = 10 for the load and the tail bias (why is this reasonable?)**

- The input pair is biased in the moderate or weak inversion to maximize efficiency and minimize power consumption.
- The load and tail are biased in the strong inversion to get high output resistance for good mirroring and good gain.

**ro of the load is five times ro of the input pair (why is this reasonable?)**

Because the load are biased in the strong inversion and ro increases as we go deeper into saturation. This improves the output resistance.

**L = 1um for the tail bias (why is this reasonable?)**

This is a long-channel device, so ro is large which results in better mirroring.

**(index 5)**

```

1 %OTA Synthesis Function
2 function OTA = designOTA(specs)
3 %Additional Specs
4 VDD = 1.8;
5
6 %load LUTs
7 load 180nch.mat;
8 load 180pch.mat;
9
10 %Input Pair
11 OTA.M1.gm = specs.GBW * specs.CL * 2 * pi;
12 % assume ro(load) = 5 * ro(input) --> ro(input) = 6/5 R_total
13 DC_Gain_mag = 10^(specs.AVDC / 20); % Convert from dB to mag
14 Rout = DC_Gain_mag / OTA.M1.gm; % Compute the equivalent output resistance of OTA (Rout)
15
16 OTA.M1.ro = (6/5)*Rout; % Complete the line to compute the ro of M1
17
18 OTA.M1.gds = 1 / OTA.M1.ro;
19 OTA.M1.VDS = VDD/3;
20 OTA.M1.gm_gds = OTA.M1.gm / OTA.M1.gds;
21 OTA.M1.gm_ID = 15; % assumption
22
23 OTA.M1.ID = OTA.M1.gm/OTA.M1.gm_ID; % Complete the line to get the current of M1
24
25 % Search for the minimum L that gives gm / gds > specified value
26 L_vector = nch.L;
27 gm_gds_vector = look_up(nch, 'GM_GDS', 'GM_ID', OTA.M1.gm_ID, 'VDS', OTA.M1.VDS, 'L', L_vector);
28
29 OTA.M1.L = min(L_vector(gm_gds_vector >= OTA.M1.gm_gds)); %Complete the line to get the minimum L that gives gm/gds >= OTA
30 % Compute ID/W to get the W value
31 OTA.M1.ID_W = look_up(nch, 'ID_W', 'GM_ID', OTA.M1.gm_ID, 'VDS', OTA.M1.VDS, 'L', OTA.M1.L);
32 OTA.M1.W = OTA.M1.ID / OTA.M1.ID_W;
33
34 %CM Load
35 OTA.M3.ID = OTA.M1.ID;
36
37 OTA.M3.ro = OTA.M1.ro * 5; %Complete the line to get the ro of the CM load
38
39 OTA.M3.gds = 1 / OTA.M3.ro;
40 OTA.M3.VDS = VDD/3;
41 OTA.M3.gm_ID = 10;
42 OTA.M3.gm = OTA.M3.gm_ID * OTA.M3.ID;
43 OTA.M3.gm_gds = OTA.M3.gm / OTA.M3.gds;
44 gm_gds_vector = look_up(pch, 'GM_GDS', 'GM_ID', OTA.M3.gm_ID, 'VDS', OTA.M3.VDS, 'L', L_vector);
45 OTA.M3.L = min(L_vector(gm_gds_vector > OTA.M3.gm_gds));
46 OTA.M3.ID_W = look_up(pch, 'ID_W', 'GM_ID', OTA.M3.gm_ID, 'VDS', OTA.M3.VDS, 'L', OTA.M3.L); %Complete the line to get the
47 OTA.M3.W = OTA.M3.ID / OTA.M3.ID_W;
48
49 % Tail bias
50 OTA.M5.L = 1; %assumption
51 OTA.M5.ID = 2 * OTA.M1.ID;
52 OTA.M5.VDS = VDD/3;
53 OTA.M5.gm_ID = 10; %assumption
54 % Get ID/W to compute W
55 OTA.M5.ID_W = look_up(nch, 'ID_W', 'GM_ID', OTA.M5.gm_ID, 'VDS', OTA.M5.VDS, 'L', OTA.M5.L);
56 OTA.M5.W = OTA.M5.ID / OTA.M5.ID_W;
57
58 % get CMIN bias value
59 OTA.M1.VGS = look_upVGS(nch, 'GM_ID', OTA.M1.gm_ID, 'VDS', OTA.M1.VDS, 'L', OTA.M1.L); %Complete the line to get the VGS of
60 OTA.M1.VG = OTA.M1.VGS + OTA.M5.VDS; %Complete the line to get the DC CM input of OTA

```

(index 6)



```

1 % OTA Design Script
2 % Write the SPECS
3 - clear all;
4 - clc;
5 - AVDC = 34; % complete the line to add the gain SPEC
6 - GBW = 100e+6; % complete the line to add the GBW SPEC
7 - CL = 500e-15; % complete the line to add the CL SPEC
8 - specs = struct('AVDC', AVDC,...
9   'CL', CL,...
10  'GBW', GBW);
11 % struct('AVDC', 50.1187,'CL', 500e-15,'GBW', 100e+6)
12 - OTA = designOTA(specs);
13 % Print the solution
14 - fprintf('**** OTA Design ****\n\n');
15 - fprintf('Input Pair:\n');
16 - fprintf('    L = %.2f um\n    W=%.2f um\n    ViCM=%.4f V\n\n',OTA.M1.L,OTA.M1.W,OTA.M1.VG);
17 - fprintf('CM Load:\n');
18 - fprintf('    L = %.2f um\n    W=%.2f um\n\n',OTA.M3.L,OTA.M3.W);
19 - fprintf('Tail Current Source:\n');
20 - fprintf('    L = %.2f um\n    W=%.2f um\n\n',OTA.M5.L,OTA.M5.W);

```

#### Command Window

```
**** OTA Design ****
```

```
Input Pair:
```

```

L = 0.28 um
W=3.01 um
ViCM=1.1928 V

```

```
CM Load:
```

```

L = 1.70 um
W=31.44 um

```

```
Tail Current Source:
```

```

L = 1.00 um
W=9.06 um

```

Comparison:

	ADT	Matlab
<b>Input pair</b>		
L	269.5 nm	0.28 um
W	2.859 um	3.01um
ViCM	1.1937	1.1928
<b>CM load</b>		
L	1.62 um	1.70 um
W	29.77 um	31.44 um

Tail current source		
L	1 um	1 um
W	8.979 um	9.06 um

The results are very close to the values obtained from ADT.

(index 7)

Netlist:


```
* Add lines here to add the input (voltage) sources
V1 4 0 1.1937 AC 0.5
V2 3 0 1.1937 AC -0.5

* circuit
* 5T OTA
M1 6 4 2 0 nch L=269.5n W=2.859u
M2 5 3 2 0 nch L=269.5n W=2.859u
M3 6 5 7 7 pch L=1.62u W=29.77u
M4 5 5 7 7 pch L=1.62u W=29.77u
M5 2 1 0 0 nch L=1u W=8.979u
CL 6 0 500f
* Current Mirror
M6 1 1 0 0 nch L=1u W=8.979u
Iref 7 1 41.888u
|
** Analysis Requests **
.op
.ac dec 10 1 10e9

.MEAS AC dc_gain max mag(V(6))
.MEAS AC BW WHEN mag(V(6)) = dc_gain/sqrt(2)
** Outputs Requests **
*.PROBE

.END
```

Simulation results:

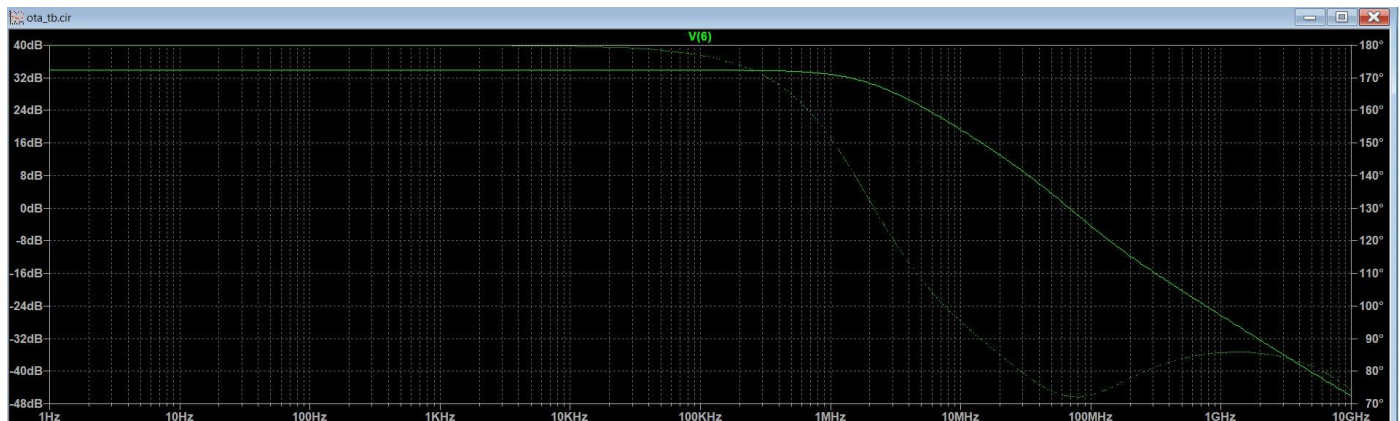

```
dc_gain: MAX(mag(v(6)))=(33.8855dB,0°) FROM 1 TO 1e+010
bw: mag(v(6))=dc_gain/sqrt(2) AT 1.90255e+006
```

Comparison table:


	Specification	ADT
AVDC	34 dB	33.8855 dB
GBW	100 MHz	94.105 MHz

Comment: the GBW spec is not met due to neglecting the parasitic capacitances during the design.


**Part (2):**

**(index 1)**

CDD of the pmos load

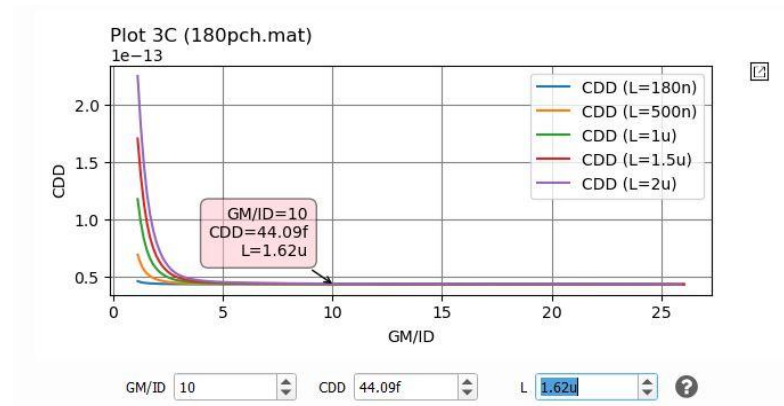


CDD of the nmos load

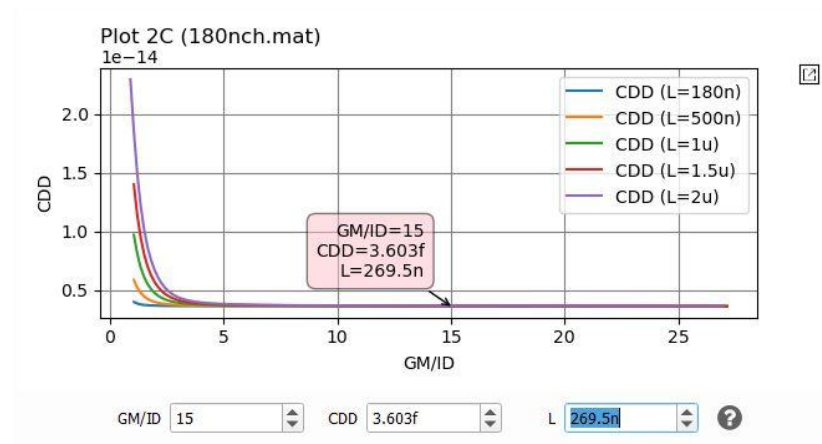


$$C_{\text{tot}} = 500\text{f} + 44.09\text{f} + 3.603\text{f} = 547.693 \text{ fF}$$

For the input pair,




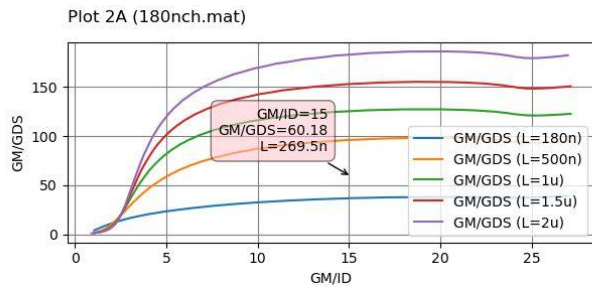


GM/ID 15 GM/GDS 60.18 L 269.5n ?

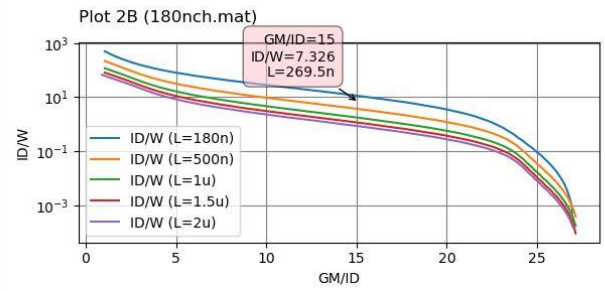

GM/ID 15 ID/W 7.326 L 269.5n ?

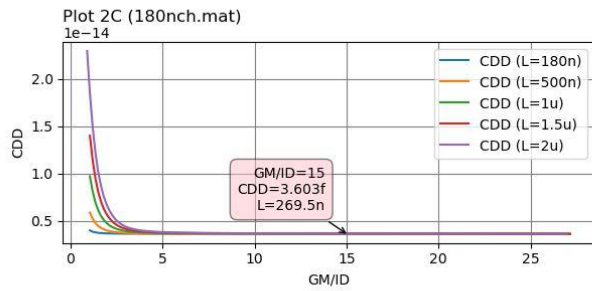


GM/ID 15 CDD 3.603f L 269.5n ?

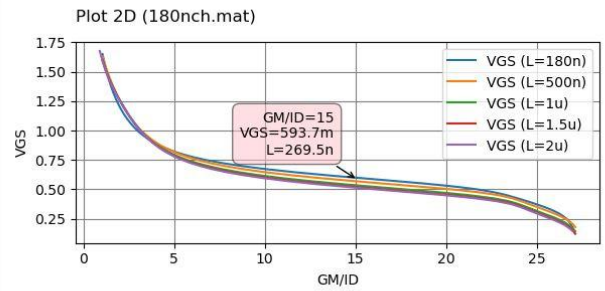


GM/ID 15 VGS 593.7m L 269.5n ?

For the load,

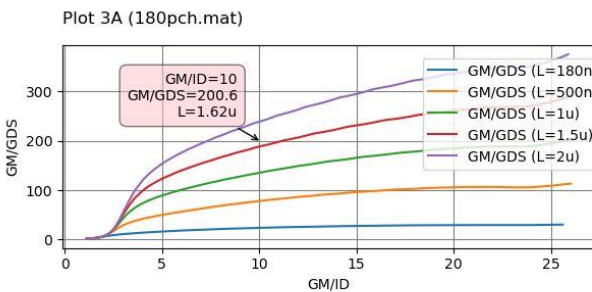


GM/ID 10 GM/GDS 200.6 L 1.62u ?

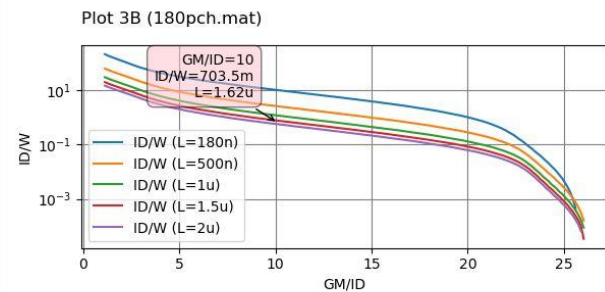


GM/ID 10 ID/W 703.5m L 1.62u ?

For the current tail,

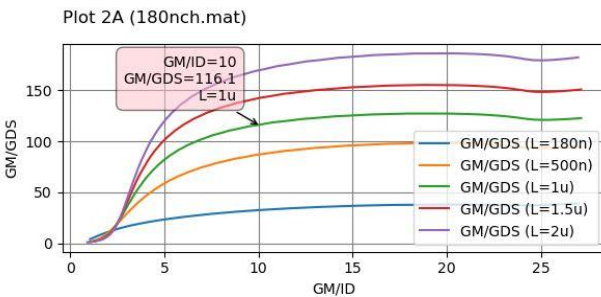

GM/ID 10 GM/GDS 116.1 L 1u ?

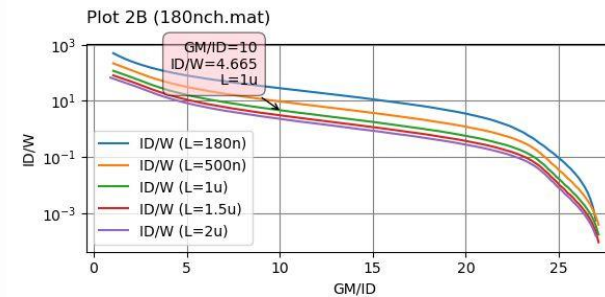

GM/ID 10 ID/W 4.665 L 1u ?

Part1

part2

Input pair		
L	269.5 nm	269.5 nm
W	2.859 um	3.1315um
ViCM	1.1937	1.1928
CM load		
L	1.62 um	1.62 um
W	29.77 um	32.61 um
Tail current source		
L	1 um	1 um
W	8.979 um	9.836 um

(index 2)

\*\*\*\* OTA Design \*\*\*\*

Input Pair:

L = 0.28 um  
W=3.30 um  
ViCM=1.1928 V

CM Load:

L = 1.70 um  
W=34.44 um

Tail Current Source:

L = 1.00 um  
W=9.93 um

**Compare the results to the results obtained in Part 1.**

	part2	part1
Input pair		
L	0.28 um	0.28 um
W	3.3 um	3.01um
ViCM	1.1928	1.1928

CM load		
L	1.70 um	1.70 um
W	34.44 um	31.44 um
Tail current source		
L	1 um	1 um
W	9.93 um	9.06 um

**Compare the results to the results obtained by ADT Device Xplore.**

	ADT	Matlab
Input pair		
L	269.5 nm	0.28 um
W	3.1315um	3.3 um
ViCM	1.1928	1.1928
CM load		
L	1.62 um	1.70 um
W	32.61 um	34.44 um
Tail current source		
L	1 um	1 um
W	9.836 um	9.93 um

**(index 3)**

```

5T OTA

* Include external file that contains MOSFET Model
.INCLUDE ee214b_hspice.sp
** Circuit Description **
|
* power supply
VDD 7 0 DC 1.8
* input

* Add lines here to add the input (voltage) sources
V1 4 0 1.1937 AC 0.5
V2 3 0 1.1937 AC -0.5


* circuit
* 5T OTA
M1 6 4 2 0 nch L=269.5n W=3.1315u
M2 5 3 2 0 nch L=269.5n W=3.1315u
M3 6 5 7 7 pch L=1.62u W=32.61u
M4 5 5 7 7 pch L=1.62u W=32.61u
M5 2 1 0 0 nch L=1u W=9.836u
CL 6 0 500f
* Current Mirror
M6 1 1 0 0 nch L=1u W=9.836u
Iref 7 1 45.8834u

** Analysis Requests **
.op
.ac dec 10 1 10e9

.MEAS AC dc_gain max mag(V(6))
.MEAS AC BW WHEN mag(V(6)) = dc_gain/sqrt(2)
** Outputs Requests **
*.PROBE

.END

```

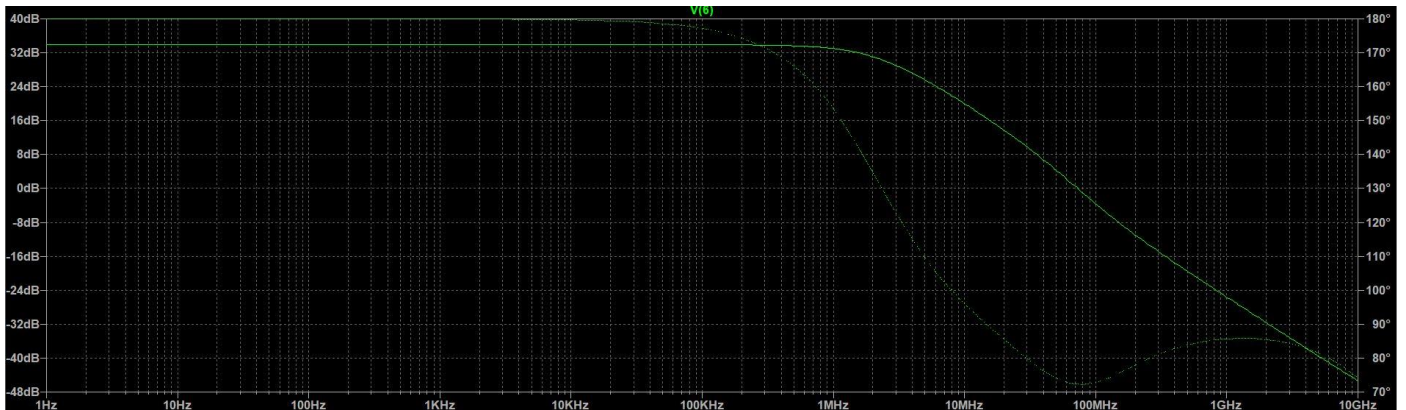

```

dc_gain: MAX(mag(v(6)))=(33.8989dB,0°) FROM 1 TO 1e+010
bw: mag(v(6))=dc_gain/sqrt(2) AT 2.0669e+006

```

Comparison table:

	Specification	ADT
AVDC	34 dB	33.8989 dB
GBW	100 MHz	102.39 MHz

Comment: the GBW spec is met after considering the parasitic capacitances.